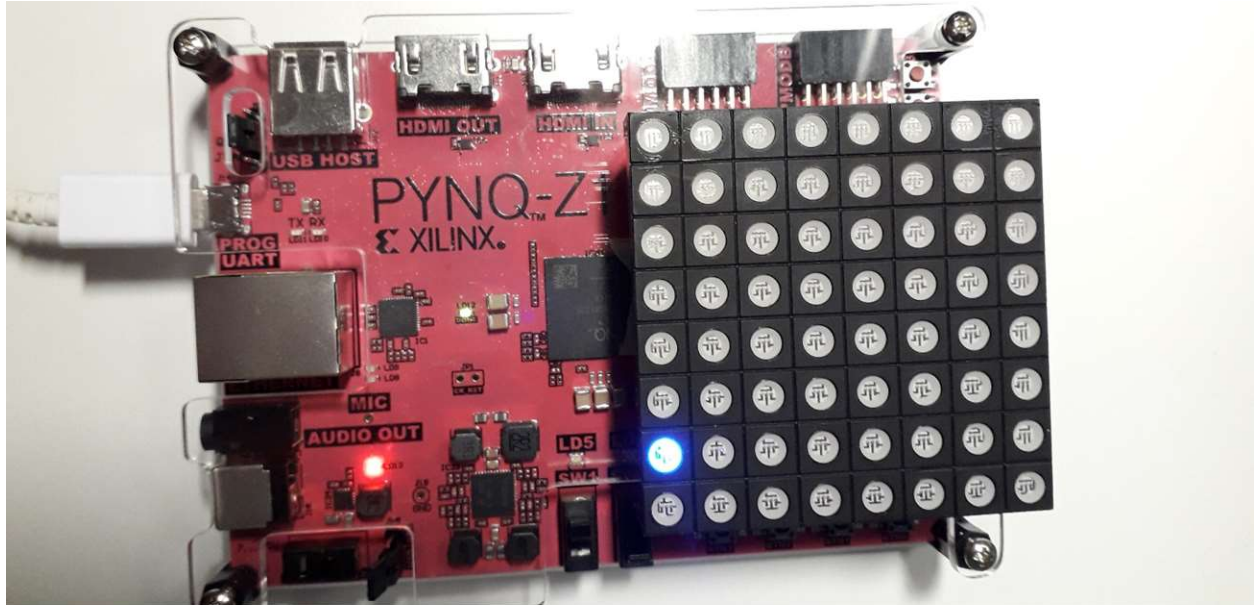



COMP exercise 4

2: Hello LED on FPGA Board

Static effect:



Interactive effect without input:

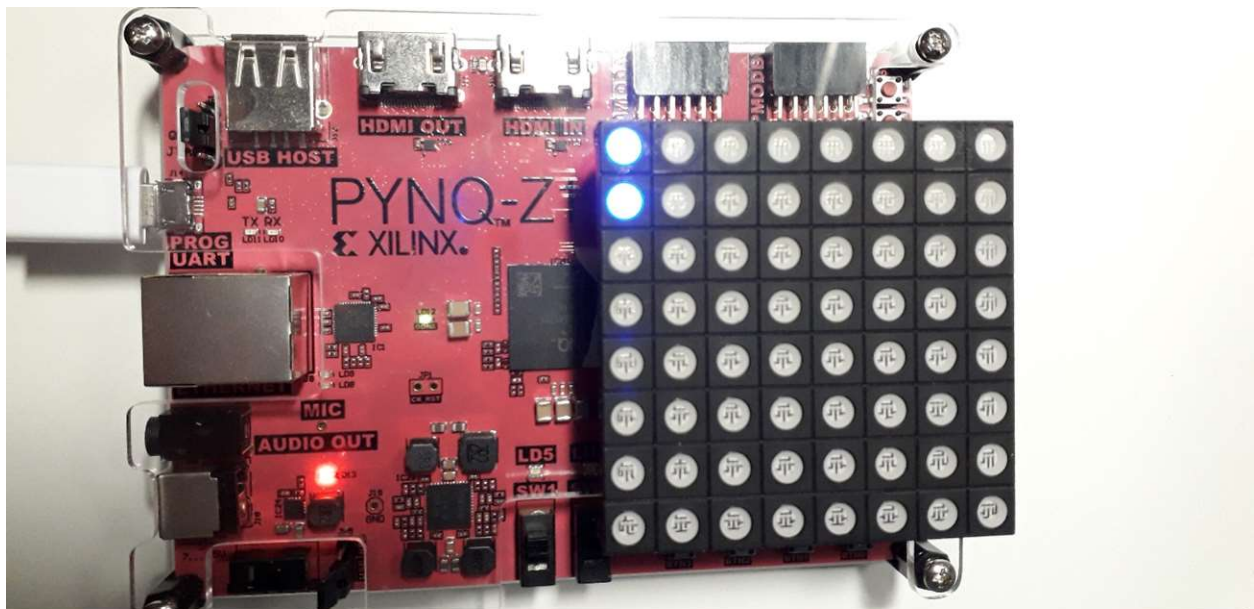

Interactive effect with input:

